

HW03

$$1. \quad 2.7 \text{ kJ} / 6.3 \text{ mW} = 2.7 \cdot 10^3 \text{ J} / 6.3 \cdot 10^{-3} \text{ W}$$

$$= 0.429 \cdot 10^6 \text{ s}$$

$$= 4.29 \cdot 10^5 \text{ seconds}$$

$$2. \quad I = 25 \text{ W} / 12 \text{ V} = 2.083 \text{ A}$$

$$57 \text{ Ah} / 2.083 \text{ A} = 27.364 \text{ hours}$$

$$3. \quad I = P/V$$

average current = $0.5 \mu\text{A} \cdot \frac{59}{60} + 154 \mu\text{A} \cdot \frac{1}{60}$

$$P = E/t$$


$$= 3.05 \mu\text{A}$$

$$I = E/V \cdot t$$

$$t = E/V \cdot I = \frac{79 \text{ J}}{2.4 \text{ V} \cdot 3.05 \cdot 10^{-6} \text{ A}}$$

$$= 1.079 \cdot 10^7 \text{ seconds}$$


4.

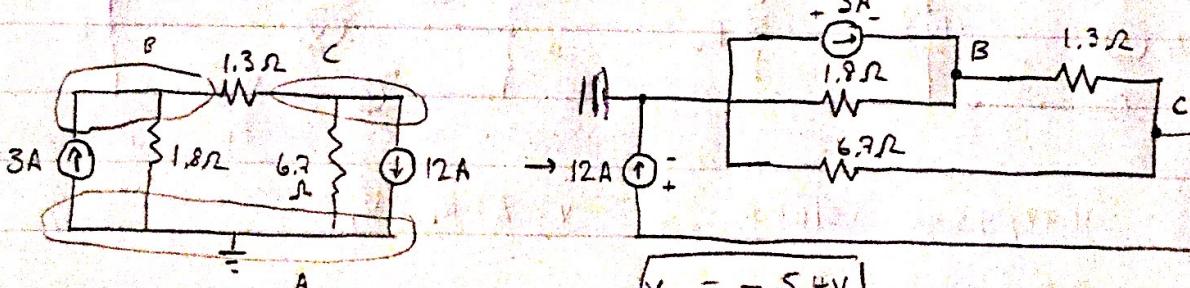

$$V_A = -5.4 \text{ V}$$

$$V_B = -40.2 \text{ V}$$

6.

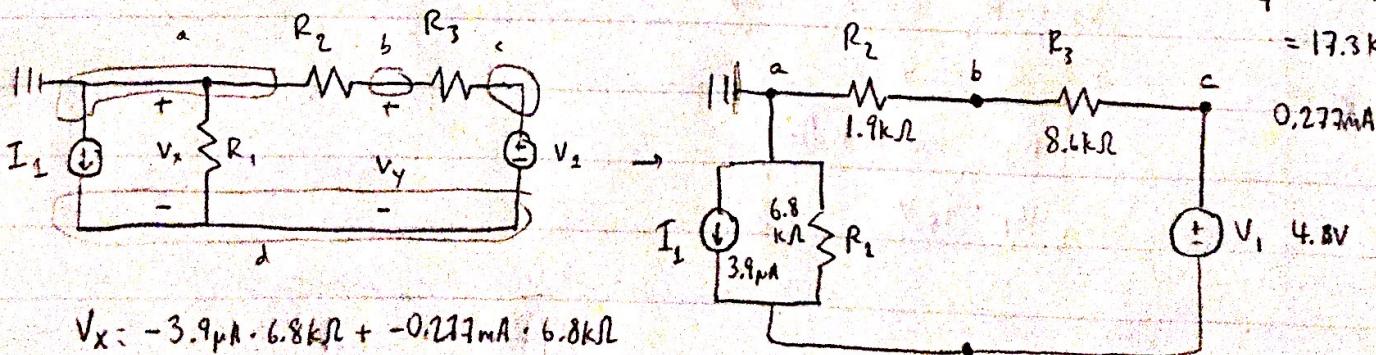

$$V_x = -3.9 \mu\text{A} \cdot 6.8 \text{ k}\Omega + -0.277 \text{ mA} \cdot 6.8 \text{ k}\Omega$$



$$= -1.9 \text{ V}$$

$$V_y = -3.9 \mu\text{A} \cdot 1.9 \text{ k}\Omega + -0.277 \text{ mA} \cdot 1.9 \text{ k}\Omega + -1.9 \text{ V}$$


$$= -2.44 \text{ V}$$

LW03

5.

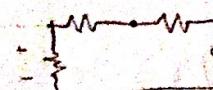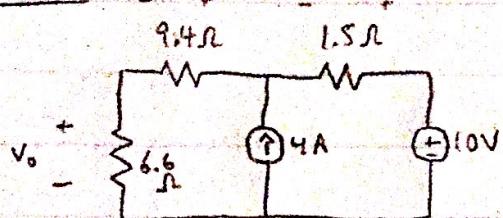

!

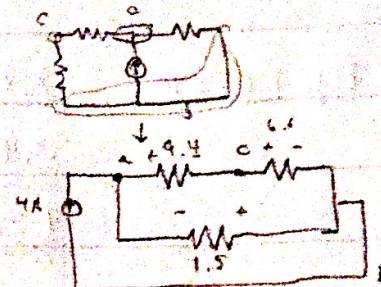

$$10V \rightarrow R_{eq} = 6.6 + 9.4 + 1.5 = 17.5\Omega$$

$$I = V/R_{eq} = 10V / 17.5\Omega = 0.57A$$

$$4A \rightarrow R_{eq} = \frac{1}{\frac{1}{4} + \frac{1}{1.5}} = 1.37\Omega$$

$$V_o = 0.57A \cdot 6.6\Omega$$

$$V_{o_1} = 3.77V$$

$$V = 1.37\Omega \cdot 4A$$

$$= 5.48V$$



$$V_{branch} = 5.48V / 2 = 2.74V$$

$$V_o = V_{o_1} + V_{o_2} = 3.77V + 1.13V = 4.9V$$

$$I_{branch} = 2.74V / 16\Omega = 0.17125A$$

$$V_{o_2} = 0.17125A \cdot 6.6\Omega = 1.13V$$

7. a)

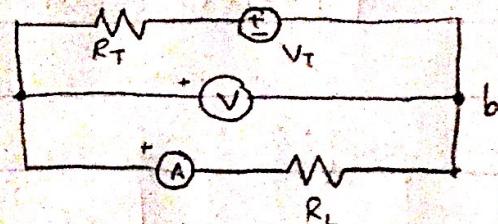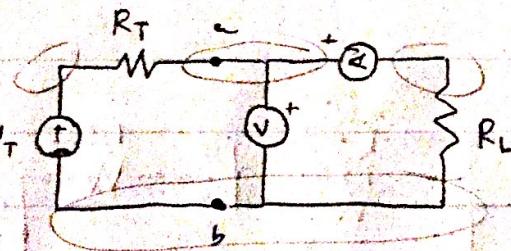

$$4.9V / 9.5mA = 0.516k\Omega$$

$$V = A \cdot R_L = V_T$$

$$9.2V / 3.8mA = 2.42k\Omega$$

$$V_T + R_T \cdot 9.5mA = 4.9V$$


$$V_T + R_T \cdot 3.8mA = 9.2V$$

$$5.7 \quad R_T = -4.3V$$

$$R_T = -0.75k\Omega$$

$$V_T = 12V$$

8. Can use a voltage divider circuit

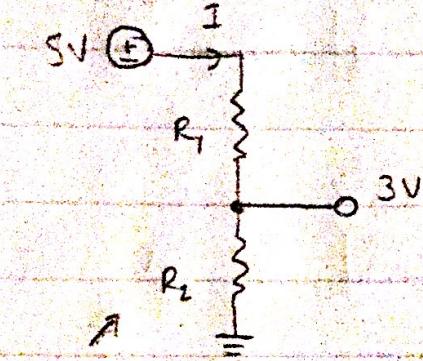

$$SV = I \cdot (R_1 + R_2)$$

$$3V = I \cdot R_2$$

$$I = \frac{SV}{R_1 + R_2}$$

$$3V = \frac{SV}{R_1 + R_2} \cdot R_2$$

$$R_1 = 0.4k\Omega$$

$$R_2 = 0.6k\Omega$$

$$5R_2 = 3(R_1 + R_2) \quad 5R_2 = 3k\Omega$$

$$R_1 + R_2 = 1k\Omega$$

$$R_2 = 0.6k\Omega$$

$$R_1 = 0.4k\Omega$$

9. $39 = 2 \cdot 16^1 + 7 \cdot 16^0 = [0x27]$

$$39 = 2^5 + 1 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 = [0b100111]$$

10. $0xff0a = 15 \cdot 16^3 + 15 \cdot 16^2 + 0 + 10$

$$= 61440 + 3840 + 10 = [65290]$$

11. $1 \cdot 2^{16} + 1 \cdot 2^{14} + 1 \cdot 2^{12} + 1 \cdot 2^8 + 1 \cdot 2^5$

$$= [0b1010100010010000]$$

16 digits