



Voltage across resister

Red: 3.3V-1.7V = 1.6V / 10mA = 160s2

Green: 3.3V-2.2V = 1.1V / LOMA = 110s

Blue: 3.3V - 2.5V = 0.8V/10mA = 801

del rgb (red, green, blue):

r = Pin (A6, mode = Pin. OPEN_DRAIN)

g = Pin (A7, mode = Pin, OPEN-DRAIN)

b = Pin (AB, mode = Pin. OPEN-DRAIN)

T= RxC Vc = Vs (1 - e-+/RC)

2.
$$V_1 = V_1 (1 - e^{-t/RC})$$

 $V_1 = 3/4 V_1$
 $3/4 = 1 - e^{-t/R \times C}$
 $= 1 - e^{-2.7s/R_1 \times 6.9mF}$
 $e^{-2.7s/R_1 \times 6.9mF} = 1/4$
 $1n(1/4) = -2.7s/6.9mF \cdot R_1$
 $6.9mF \cdot R_1 = -2.7s/1n(1/4)$
 $R_1 = -2.7s/1n(1/4) \cdot 6.9mF$
 $= 282.3.D$

$$V_1 = V_H \times e^{-t/RC} = \frac{1}{3} V_H$$

$$e^{-6.3s/R \cdot 6.9mF} = \frac{1}{3}$$

$$-6.3s/R_2 \cdot 6.9mF = \ln(1/3)$$

$$R_2 = -6.3s/\ln(1/3) \cdot 6.9mF$$

= [831.1 1]

$$R_1 = 282.3 \Omega$$
 $R_2 = 831.1 \Omega$

3. no finger
$$r = 50\%$$
 $T_1 = -(\ln \frac{1}{2})/500k\Omega \cdot 4.9 pF = 282917s$ finger $r = 50\%$ $T_1 = -(\ln \frac{1}{2})/500k\Omega \cdot 4.9 pF \cdot 1.2 = 235764s$ no finger $r = 60\%$ $T_1 = -(\ln \frac{3}{5})/500k\Omega \cdot 4.9 pF = 208500s$ finger $r = 60\%$ $T_1 = -(\ln \frac{3}{5})/500k\Omega \cdot 4.9 pF \cdot 1.2 = 173750s$

$$\ln r = -T_1/R \cdot C$$

$$T_1 = -(\ln r)/(R \cdot C)$$

no finger
$$r=502$$
 $T_1+T_2=282917\cdot 2=565834$ seconds

finger $r=502$ $=235764\cdot 2=471528$ seconds

no finger $r=60$ $=208500s+-\ln(2/s)/500kl\cdot 4.9pF=582496$ seconds

finger $r=60$ $=173750s+-\ln(2/s)/500kl\cdot 4.9pF=485419$ seconds